

**DESIGN BRIEFS**Cycle  
skipping

nected to a normally closed pushbutton switch) can clear a fault on U1 or supply a manual reset. An internal pull-up to V<sub>CC</sub> eliminates the need for an external pull-up resistor. Replacing the pushbutton switch with an interlock or single-pole, single-throw (SPST) switch supplies a power-disconnect signal, which can implement a chassis-intrusion interlock or allow a technician to power-down the unit before swapping circuit cards. Because U2's push-pull output can't be directly OR-connected with other signals joined to U1's ON pin, Q2 is added to create an OR-able open-drain connection.

A temperature switch (U3) adds thermal protection, and its open-drain output can be linked either directly (wire-OR'd) to other signals on U1's ON pin, or separately, back to the microprocessor. With its TO220 package option, U3 can be bolted to a heatsink or surface-mounted (SOT23 option) close to known heat-generating sources such as R1, Q1, or the main load.

In this circuit, U3 provides circuit protection by issuing a power-disconnect signal when the circuit temperature becomes critical. A low-power linear regulator (U4) supplies 5 V to the low-voltage components U2 and U3, but U4 isn't meant to provide system power to the load. **ED Online 5396**

**MARK PEARSON** is senior FAE for Maxim Integrated Products. He received a BEE from the University of Minnesota Institute of Technology, Minneapolis.

**DESIGN BRIEFS WANTED**

We'll pay you \$100 for every **Design Brief** that we publish.

You can submit your ideas for **Design Briefs** via:

- E-mail: [dbs@penton.com](mailto:dbs@penton.com)

- Postal mail:

**Design Briefs Editor**

Electronic Design  
45 Eisenhower Dr., 5th Floor  
Paramus, NJ 07562

Go to [www.elecdesign.com](http://www.elecdesign.com) for our submission guidelines.

**DESIGN BRIEFS Innovative Designs from Readers**

# Increase Common-Mode Range For Fully Differential Amplifiers

*Art Kay*


*kay\_art@ti.com • Texas Instruments, Tucson, Ariz.*

Fully differential amplifiers have grown in popularity because of their low distortion, excellent noise rejection, and the simplicity of interfacing them with differential analog-to-digital converters (ADCs). This application shows how to increase the common-mode range of a fully differential amplifier by using a few external resistors (Fig. 1).

The circuit uses a voltage-divider technique to reduce the voltage at the inputs of the differential amplifier. This method was adapted from a technique employed on a monolithic instrumentation amplifier (INA148) for use with the fully differential amplifier. Implementing the given configuration, the amplifier's common-mode range is approximately  $\pm 90$  V, with a differential gain of approximately 1.0. Even wider common-mode ranges could be achieved using a larger R1/R2 ratio.

Three important considerations when executing this topology are determining the gain, the maximum common-mode range, and the common-mode rejection. Modeling the differential amplifier as a voltage-controlled voltage source is the basis of the analysis (Fig. 2).

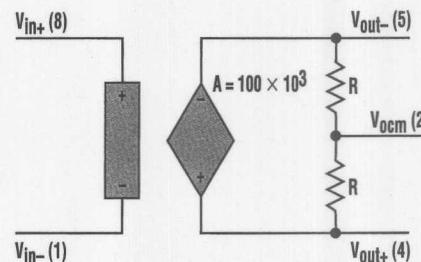Assuming the resistors are equivalent in both halves of the amplifier simplifies the analysis (i.e., R1a = R1b = R1). Equation 1 gives the gain of the amplifier.



**2. For analysis purposes, the differential amplifier is modeled as a voltage-controlled voltage source.**

$$V_{\text{OUT}} = \frac{(V_{\text{IN}1} - V_{\text{IN}2}) \times (R_4 R_3 + R_3 R_2 + R_4 R_2)}{(R_1 R_4)} \quad (1)$$

This simplified equation will always yield a zero common-mode output. Performing a more detailed analysis that uses unique values for all resistances produces a far more complex equation.


**ED Online 5395**

**ART KAY**, a test development engineer, received an MSEE from the Georgia Institute of Technology.
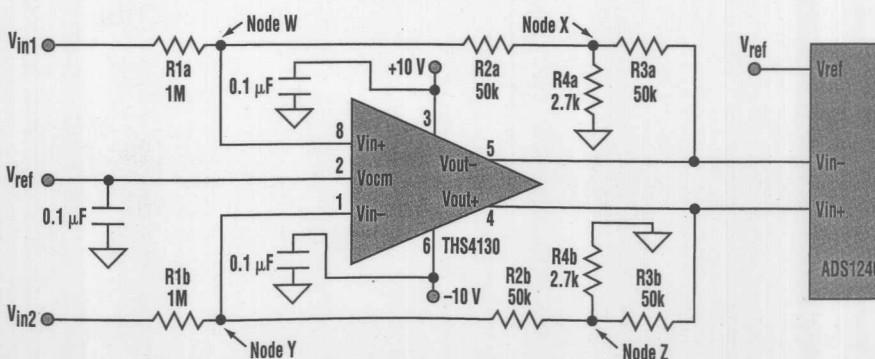
## DRILLDEEPER: 5394

Equations for determining common-mode performance... Plus downloadable PDF of derivation

[www.elecdesign.com](http://www.elecdesign.com)



**1. Resistors R1 and R2 form a voltage divider that increases this differential amplifier's common-mode range to approximately  $\pm 90$  V.**